

This material may be  
protected by copyright  
law (Title 17, U.S. Code)

# Quasi-Complementary Transistor Amplifier

**SUMMARY** — Transistorized phonograph amplifier uses a quasi-complementary output circuit to provide 6 watts output with less than 1-percent distortion at midfrequencies. Input signal passes through three preamplifiers and a predriver stage before reaching the quasi-complementary output stage. Output feeds directly to loudspeaker voice coil. Operation is satisfactory over temperature range from 0 to 50 C

By H. G. LIN\*

Research Engineer  
RCA Laboratories  
Princeton, N. J.

**O**PERATING between a variable-reluctance pickup and a conventional 16-ohm loudspeaker, the amplifier to be described has a frequency response flat within 1½ db from 30 to 15,000 cps and tone controls with boost and cut for bass and treble.

A discussion of some considerations in a transistor phonograph amplifier precedes the description of the circuit.

## Distortion

Distortion in a transistor amplifier is usually due to variations with current of either the current-amplification factor, the transconductance or both. When driving a grounded-emitter transistor amplifier stage from a current source (generator  $Z \gg \text{input } Z$ ) distortion depends on the variation in collector-to-base current-amplification factor. At high currents, the current-amplification factor usually diminishes.<sup>1</sup>

When a grounded-emitter transistor amplifier stage is driven from a voltage source, (generator  $Z \ll \text{input } Z$ ), distortion may arise from the dependence of transconductance on base-to-emitter voltage. This nonlinearity in transconductance may be caused by too low or too high an operating cur-


rent.<sup>2</sup> Either of these distortions can be reduced by negative feedback.

## Frequency Response

A system employing an RCA SPC-1 variable reluctance pickup and the RIAA recording characteristic requires high and low-frequency equalization in the reproducing amplifier. High-frequency equalization can be obtained by making the amplifier input re-

sistance equal to 7,000 ohms. Since the common-emitter transistor input resistance is generally less than 7,000 ohms, the input resistance can be increased by adding resistance to either the base or emitter circuit.

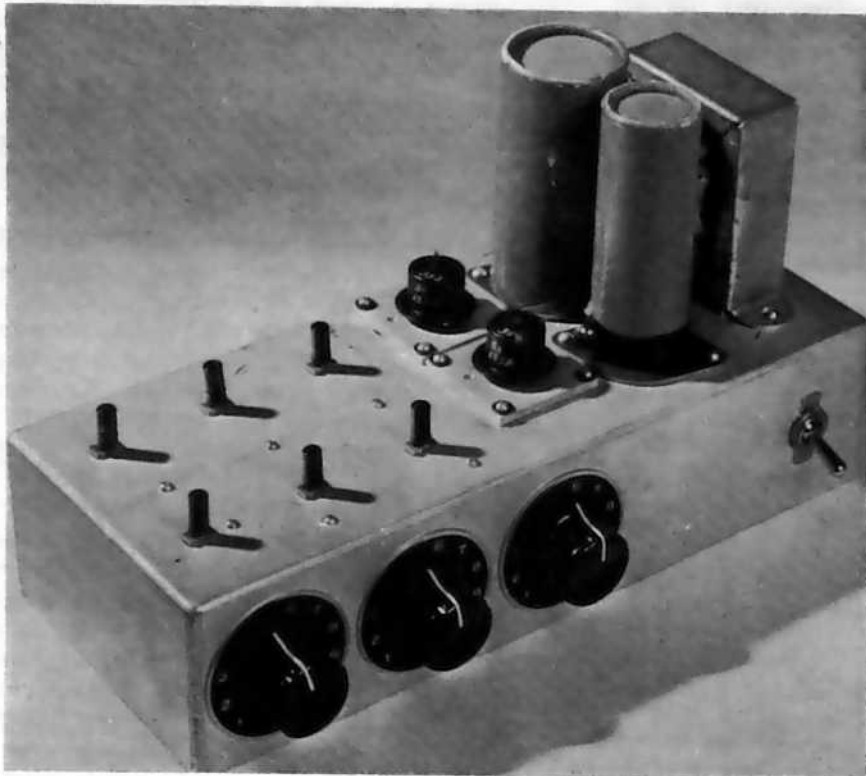If a resistance,  $R_B$  is connected in series with the emitter, the input resistance is increased by approximately  $\beta R_B$  where  $\beta$  is the collector-to-base current-amplification factor. Here the input re-



Compact transistorized amplifier uses 12-watt filament transformer, with rewind secondary, as power transformer

\*Now with CBS-Hytron, Lowell, Massachusetts.



will not be diverted into  $R_1$ .

For the negative half cycle the input resistance between  $B$  and  $A$  is approximately  $r_b + \beta r_e$ , where  $r_b$  and  $r_e$  are the base lead resistances of  $Q_6$  and  $Q_7$ . For the positive half-cycle, the input resistance is approximately  $r_b$ , the base lead resistance of  $Q_6$ . For perfect balance, these input resistances could be made equal by connecting  $R_8$  in series with the emitter of  $Q_6$ , as shown. However,  $R_8$  can usually be dispensed with if  $R_1$  is large.  $R_2$  should be much greater than  $R_1$ , since the former is in shunt with the latter.

### Complete Circuit

The complete schematic diagram of the amplifier is shown in Fig. 2. There are six stages, consisting of the quasi-complementary driver-output circuit, a predriver and three preamplifiers. Transistor  $Q_1$  is an experimental transistor similar to the 2N104 but with somewhat higher collector-to-base current-amplification factor  $\beta \cong 85$ . Transistors  $Q_4$  and  $Q_5$  are experimental *pnp* transistors with characteristics similar to those of the 2N109 but with a collector breakdown voltage of over 40 v. Experimental *nnp* transistor  $Q_6$  has characteristics complementary to that of  $Q_5$ . Both  $Q_7$  and  $Q_8$  are *pnp* power transistors.

In the first stage, an unbypassed resistor  $R_1$ , connected in series with the emitter reflects an input resistance of 7,000 ohms at the base. The base-to-emitter bias is furnished by  $R_1$  and  $R_2$  connected between collector and base. These resistors with collector resistor  $R_3$  constitute a d-c feedback circuit for stabilizing the operating point against ambient temperature variations.<sup>5</sup> Similar biasing arrangements are used in the next two stages. Bypassing capacitor  $C_1$ , connected to the junction of  $R_1$  and  $R_2$ , presents degeneration. Resistor  $R_4$  linearizes the transconductance of  $Q_2$  and reflects an input resistance of approximately 800 ohms.

### Predriver

The predriver  $Q_3$ , operates class A. The output is directly coupled to the input of the driver. Resistors

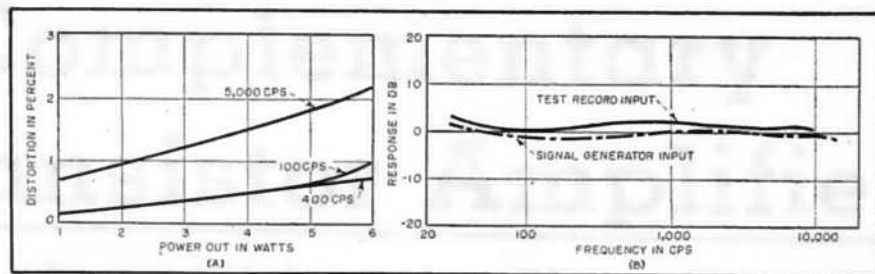


FIG. 3—Curves show distortion with change in power out (A) and frequency response for two input conditions (B)

$R_6$ ,  $R_9$  and  $R_{10}$  form the return path for the d-c collector current of  $Q_4$ . The flow of d-c through  $R_{10}$  creates a forward base-to-emitter bias for drivers  $Q_5$  and  $Q_6$ , which eliminates crossover distortion. The required bias voltage to maintain class B operation of the driver decreases with increase in temperature. The thermistor, in parallel with  $R_{10}$ , provides this bias.

Since the voltages at the emitters of  $Q_5$  and  $Q_6$  follow closely the voltage at the collector of  $Q_4$ , any change in collector current will upset the balance of the subsequent stages. To hold  $Q_4$  collector current constant, emitter resistance  $R_9$  and negative d-c feedback through  $R_7$  are used.

### Feedback

Since the output is capacitively coupled to the 16-ohm load, the d-c power supply need not have a center tap. Negative feedback is applied from the hot side of the loudspeaker voice coil to the base of  $Q_4$  through  $R_{11}$  and  $R_7$ .  $C_2$  is connected in parallel with  $R_{11}$  to give a step-response in the feedback loop for stability. The use of  $R_{12}$  between emitters of the drivers helps to temperature stabilize the driver stage. Resistor  $R_{13}$  also serves this purpose by reducing the external d-c resistance between base and emitter to a low value.

The peak a-c voltage swing at the collectors of the transistors  $Q_4$  through  $Q_6$  is nearly equal to the supply voltage. Since the no-signal supply voltage is 40 v, the transistor breakdown-voltage must be in excess of this.

### Output

The envelope of the power-output transistor is electrically connected

to the collector and must be insulated from the main chassis. The envelope should also have good thermal contact with the main chassis to remove the heat generated in the transistor. For these purposes, an anodized aluminum plate which insulates electrically but conducts thermally, is sandwiched between the power transistor and the main chassis.

### Performance

Amplifier distortion is shown in Fig. 3A. Note that the distortion for 100 cps and 400 cps is below 1 percent at six watts, whereas the distortion for 5,000 cps is somewhat higher because of the reduction in current gain and negative feedback.

The frequency response is shown in Fig. 3B. Measurements were made with the tone controls at mid-position and the volume control at maximum. The upper curve shows the response to an RIAA test tone record using the SPC-1 variable reluctance pickup. The lower curve was taken with a signal generator whose output voltage was adjusted to conform with RIAA characteristics and connected in series with a variable reluctance pickup head. At other volume control settings, the frequency response does not vary appreciably.

### REFERENCES

- (1) W. M. Webster, On the Variation of Junction Transistor Current Amplification Factor With Emitter Current, *Proc IRE*, 42, June 1954.
- (2) L. J. Glacchetto, Power Transistor For Audio Output Circuits, *ELECTRONICS*, 27, Jan. 1954.
- (3) D. D. Holmes, T. O. Stanley and L. A. Freedman, A Developmental Pocket-size Broadcast Receiver Employing Transistors, *Proc IRE*, 44, June 1955.
- (4) A. Aronson, Transistor Audio Amplifiers, "Transistor I," p 515, RCA Laboratories, 1956.
- (5) H. C. Lin and A. A. Barco, Temperature Effects in Circuits Using Junction Transistors, "Transistor I," p 369, RCA Laboratories, 1956.